

I2C Bus Pullup Resistor Calculation

Rajan Arora

ABSTRACT

Pullup resistor calculation for I2C interface is a commonly asked question. In this application note we show how to use simple equations for this calculation.

Contents

1	Introduction	1
2	Pullup Resistor Calculation	2
3	Speed Versus Power Trade-off	4
4	Example	4

List of Figures

1	Application Example Showing I2C Communication Between the Different IC's on a System and With Pullup Resistors on I2C Bus	2
2	Minimum Pullup Resistance [R_p (min)] vs Pullup Reference Voltage (V_{CC})	3
3	Maximum Pullup Resistance [R_p (max)] vs Bus Capacitance (C_b)	3

List of Tables

1	Parametrics from I2C specifications	3
---	---	---

Trademarks

1 Introduction

I2C communication standard is the mostly widely used inter-chip communication standard in today's electronic systems. It is an open-drain/open-collector communication standard which implies integrated circuits (IC's) with different voltage supply rails can be connected for communication. Pullup resistors need to be connected from the I2C lines to the supply to enable communication as shown in [Figure 1](#). The pullup resistors pull the line high when it is not driven low by the open-drain interface. The value of the pullup resistor is an important design consideration for I2C systems as an incorrect value can lead to signal loss. In this article we show the simple equations for the pullup resistor calculation which the system designer can use to do quick calculations for their design.

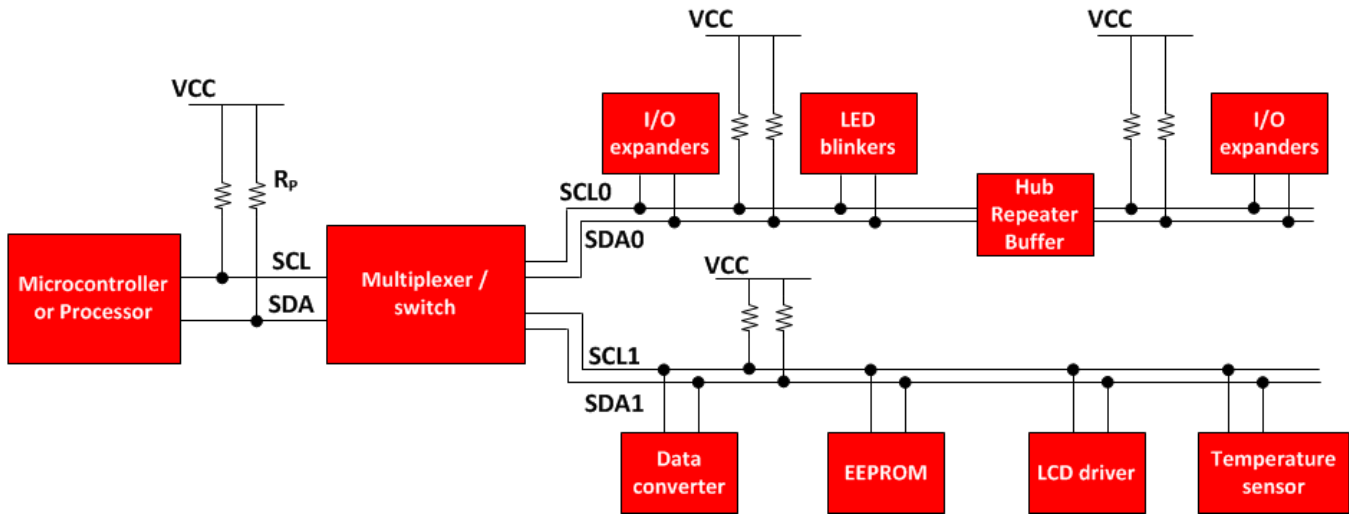


Figure 1. Application Example Showing I2C Communication Between the Different IC's on a System and With Pullup Resistors on I2C Bus

2 Pullup Resistor Calculation

A strong pullup (small resistor) prevents the I2C pin on an IC from being able to drive low. The V_{OL} level that can be read as a valid logical low by the input buffers of an IC determines the minimum pullup resistance [$R_P(\min)$]. $R_P(\min)$ is a function of V_{CC} , $V_{OL}(\max)$, and I_{OL} :

$$R_P(\min) = \frac{(V_{CC} - V_{OL}(\max))}{I_{OL}} \quad (1)$$

The maximum pullup resistance is limited by the bus capacitance (C_b) due to I2C standard rise time specifications. If the pullup resistor value is too high, the I2C line may not rise to a logical high before it is pulled low. The response of an RC circuit to a voltage step of amplitude V_{CC} , starting at time $t = 0$ is characterized by time constant RC. The voltage waveform can be written as:

$$V(t) = V_{CC} \times \left(1 - e^{\frac{-t}{RC}}\right) \quad (2)$$

For $V_{IH} = 0.7 \times V_{CC}$:

$$V_{IH} = 0.7 \times V_{CC} = V_{CC} \times \left(1 - e^{\frac{-t_1}{R_P \times C_b}}\right) \quad (3)$$

For $V_{IL} = 0.3 \times V_{CC}$:

$$V_{IL} = 0.3 \times V_{CC} = V_{CC} \times \left(1 - e^{\frac{-t_2}{R_P \times C_b}}\right) \quad (4)$$

The rise time for the I2C bus can be written as:

$$t_r = t_2 - t_1 = 0.8473 \times R_P \times C_b \quad (5)$$

The maximum pullup resistance is a function of the maximum rise time (t_r):



$$R_P(\max) = \frac{t_r}{(0.8473 \times C_b)} \quad (6)$$

where parametrics from I2C specifications are listed in [Table 1](#).

Table 1. Parametrics from I2C specifications

Parameter		Standard Mode (Max)	Fast Mode (Max)	Fast Mode Plus (Max)	Unit
t_r	Rise time of both SDA and SCL signals	1000	300	120	ns
C_b	Capacitive load for each bus line	400	400	550	pF
V_{OL}	Low-level output voltage (at 3 mA current sink, $V_{CC} > 2$ V)	0.4	0.4	0.4	V
	Low-level output voltage (at 2 mA current sink, $V_{CC} \leq 2$ V)	–	$0.2 \times V_{CC}$	$0.2 \times V_{CC}$	V

The R_p (min) is plotted as a function of V_{CC} in Figure 2. The R_p (max) is plotted as a function of C_b in Figure 3 for standard-mode and fast-mode I2C.

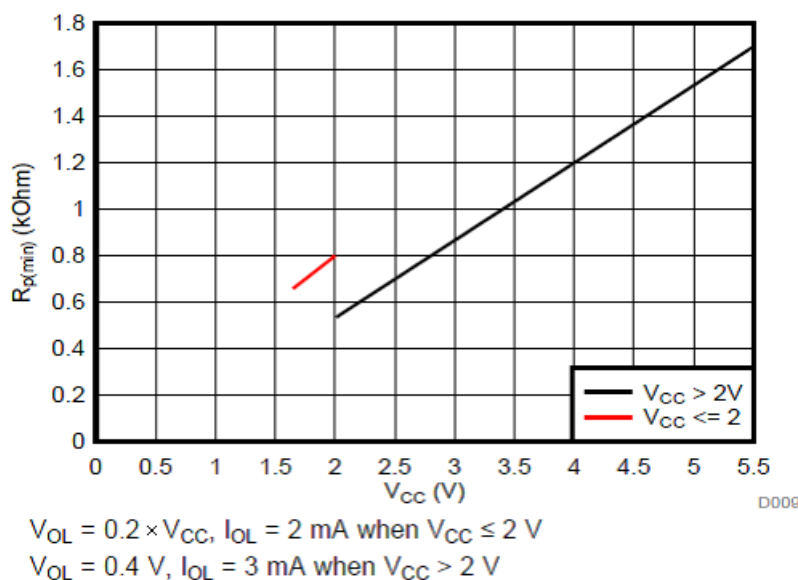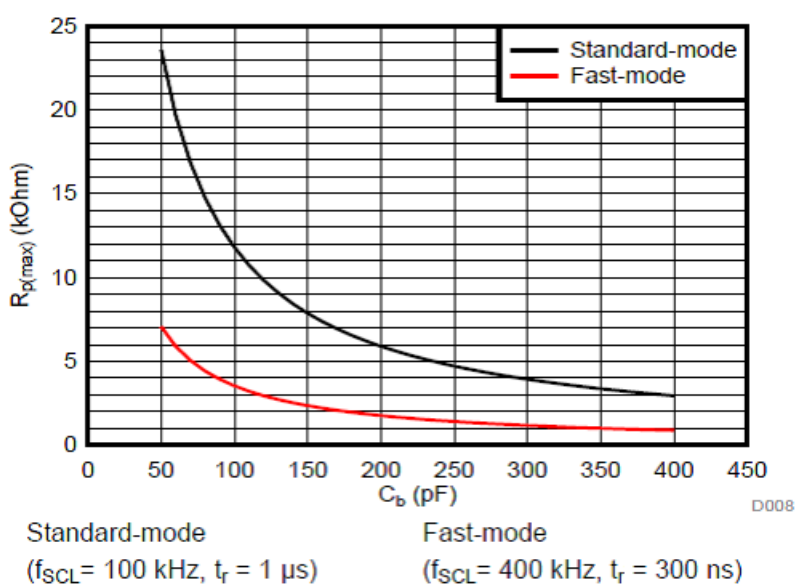
Figure 2. Minimum Pullup Resistance [R_p (min)] vs Pullup Reference Voltage (V_{CC})

Figure 3. Maximum Pullup Resistance [R_p (max)] vs Bus Capacitance (C_b)

3 Speed Versus Power Trade-off

Once the minimum and maximum value of the pullup resistor has been selected, the decision for the value of resistor can be made based on trade-off between the speed and power budget. A smaller resistor will give a higher speed because of smaller RC delay, and a larger resistor will give lower power consumption.

4 Example

For Fast-mode I2C communication with the following parameters, calculate the pullup resistor value.

$$C_b = 200 \text{ pF}, V_{CC} = 3.3 \text{ V}$$

Solution:

Taking the values from [Table 1](#):

$$R_P(\text{max}) = \frac{t_r}{(0.8473 \times C_b)} = \frac{(300 \times 10^{-9})}{(0.8473 \times 200 \times 10^{-12})} = 1.77 \text{ k}\Omega \quad (7)$$

$$R_P(\text{min}) = \frac{V_{CC} - V_{OL}(\text{max})}{I_{OL}} = \frac{(3.3 - 0.4)}{(3 \times 10^{-3})} = 966.667 \text{ }\Omega \quad (8)$$

Therefore, we can select any available resistor value between 966.667 Ω and 1.77 k Ω . The value of the pullup resistor can be selected based on the trade-off for the power consumption and speed.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated